
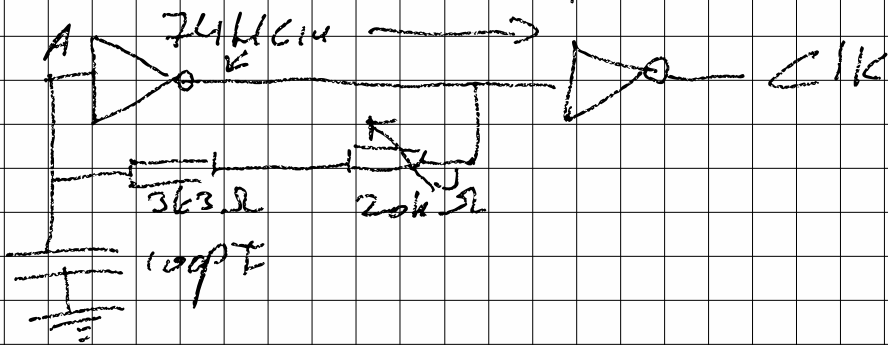


Procedure

Oscillator:

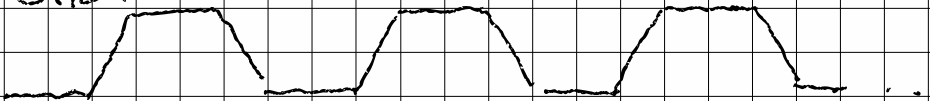


CLK:



Duty cycle variable by 20k Ω ~~resistor~~

Input A_i

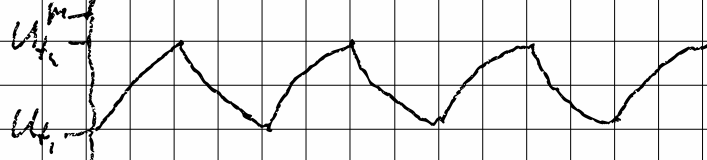

or


Basically Schmitt Trigger, explained in assignment.

Pulse Generator:

Only pulse Q0 & Q5


Then 2 Smith triggers to work as voltage follower to protect the pulse generator from drawing too much current.

Power Switch:

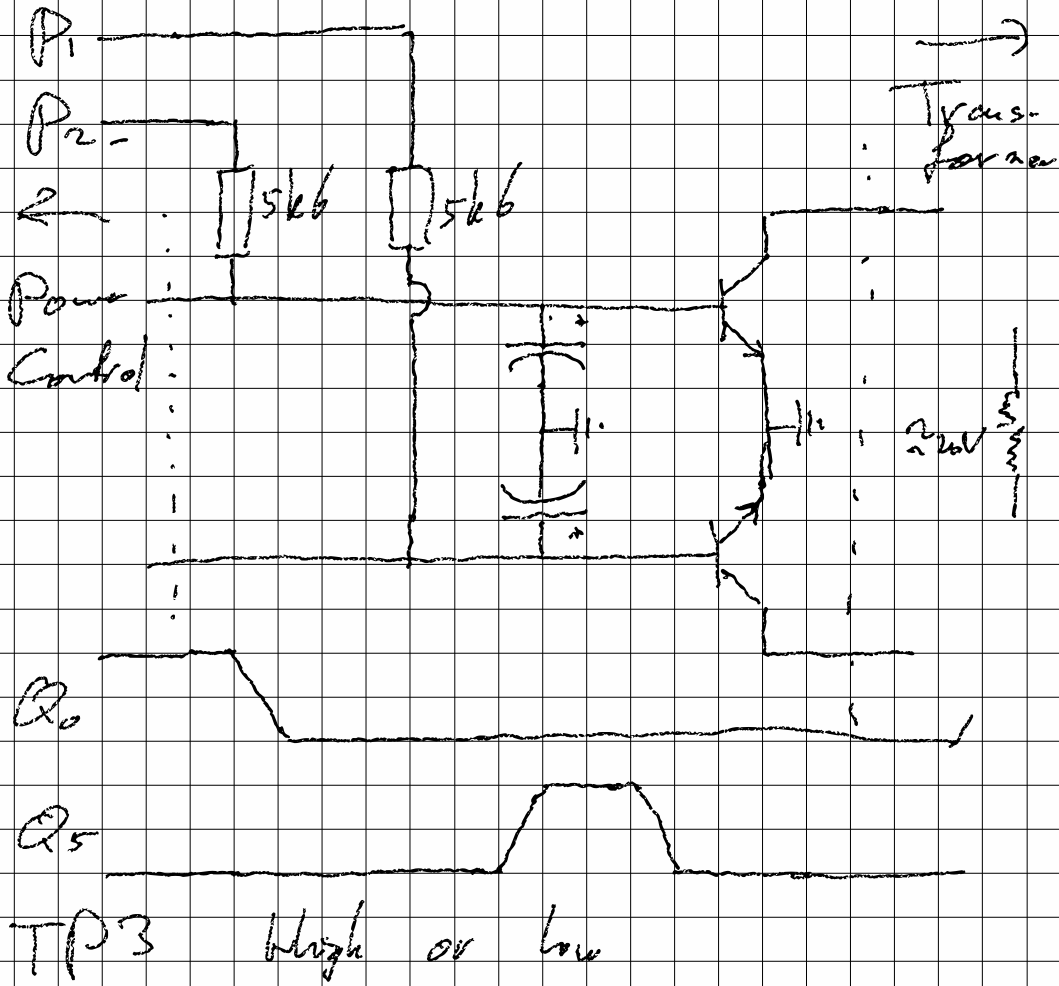


Transformer


Voltage

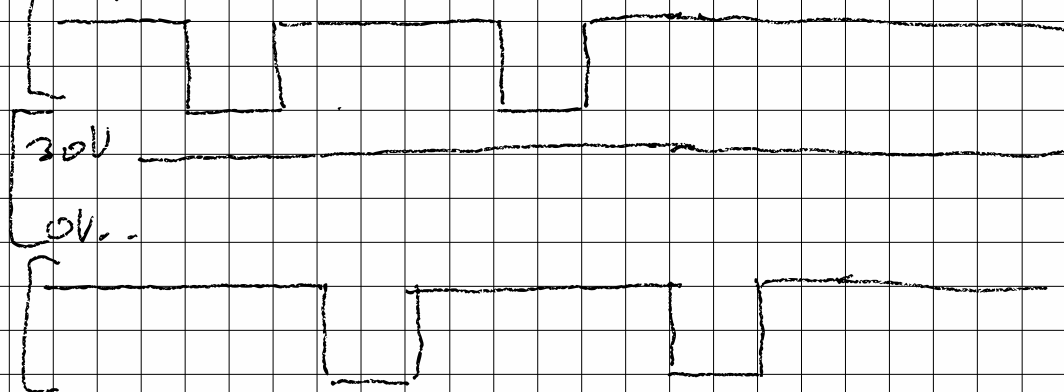


Current

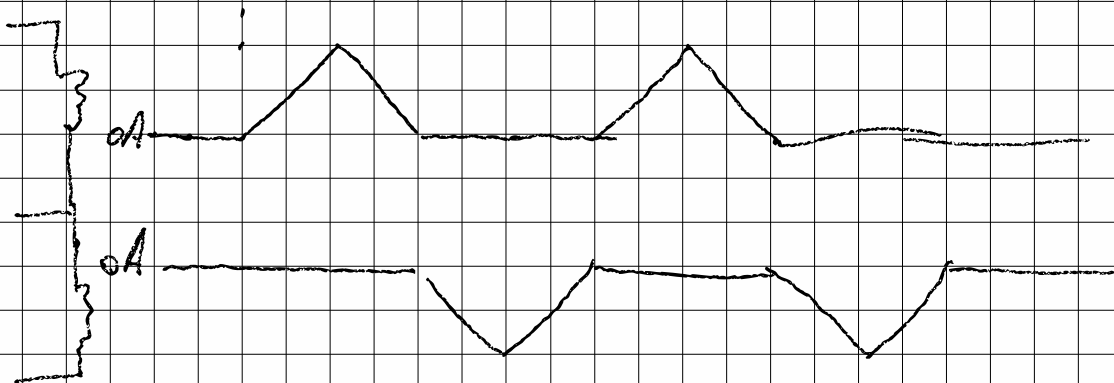


other side

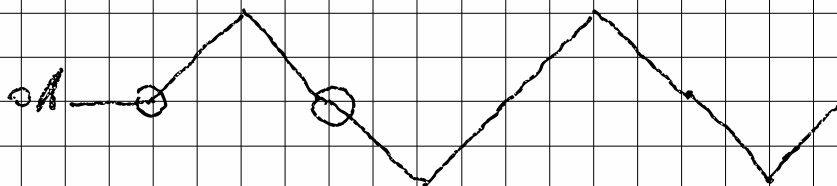


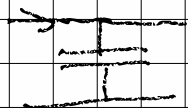

Transformer Continue

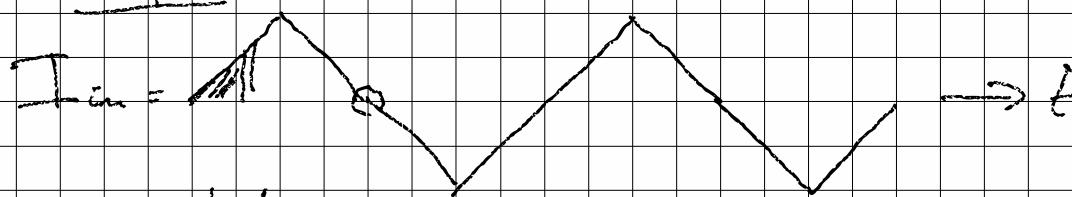
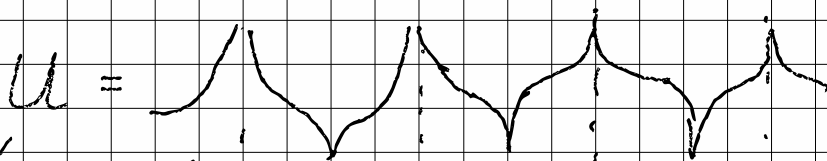
$$I = C \frac{dU}{dt} \Rightarrow \int I dt = C dU$$



± stabilization around $\pm 0V$

NPN transistor collector breakdown current:

<http://industrial-electronics.com/DC-part3.html>

→ ± load, the current peaks.

$$U = L \frac{dI}{dt}$$

$$C = \frac{Q}{U}$$

$$CU = Q$$

Voltage Multiplier /
Voltage Cascade

Lab 4:

$C_1 = 470 \text{ pF}$

$C_3 = \text{N.C.}$

2.3 Scope - ① / 1

1 : TCP

2 : OSC-OP

Scope 2: Max freq

Scope 3: Min freq

2.4 Scope 4: 1: Pulse 0
2: OSC-OP


Scope 5: 1: pulse 1
2: OSC-OP

Scope 6: 1: pulse 1
2: pulse 0

2.5 $U^+ = 0 \text{ V}$

Scope 7: 1: Feedback Y_0
2: op-amp Y_0

$U^+ = 1.5 \text{ V}$

Scope 8: 1: 

2.5

Scope - 9: 1: opamp o/p
 Scope - 10: 2: J_D: Mon
 Gain min = 1
 Scope - 11: 1:
 Gain Max

Scope - 12: 2V input
 Feedback.

2.6. Scope - 13: 1: opamp o/p
 2: TP 3
 Pot 100%
 Scope - 14:
 pot 0%
 } Very careful
 in know

Scope - 15: 1: V_{ref} opamp o/p = 4.6V
 (U₃ A) pin 3
 $V^+ = V^- = GND$
 $V_o \approx 70 mV$

2.7 scope_16: 1: TP3
Vref = -5V 2: TP2

Increase Vref
scope_17/10

2.8 scope_18: 1: TP2
2: TP1
Traf. resonance

~~2.9~~ 3.2 3.176 V
with 1/1000

Make it clean (CLK)

3.222 V (scope_20)

3.3 R6 ref Vref

$\frac{1}{1000} V_0 = 3.759 V$ scope 21

$\frac{1}{1000} V_{low} = 157.7 mV$